

Integrated Circuits for Communication



**Berkeley**

## Distortion Analysis

Prof. Ali M. Niknejad


U.C. Berkeley

Copyright © 2016 by Ali M. Niknejad

March 7, 2016

## The Origin of Distortion

# Introduction to Distortion

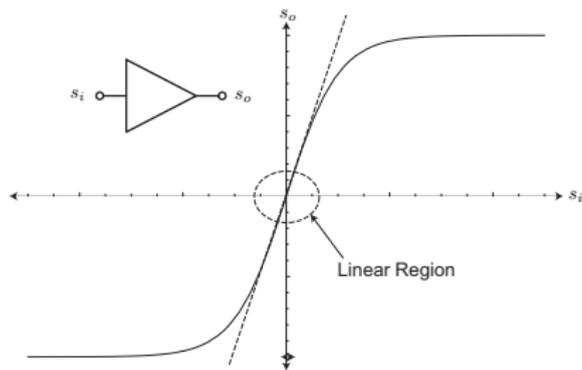


- Up to now we have treated amplifiers as small-signal linear circuits. Since transistors are non-linear, this assumption is only valid for extremely small signals.
- Consider a class of memoryless non-linear amplifiers. In other words, let's neglect energy storage elements.
- This is the same as saying the output is an instantaneous function of the input. Thus the amplifier has no memory.

# Distortion Analysis Assumptions


- We also assume the input/output description is sufficiently smooth and continuous as to be accurately described by a power series

$$s_o = a_1 s_i + a_2 s_i^2 + a_3 s_i^3 + \dots$$

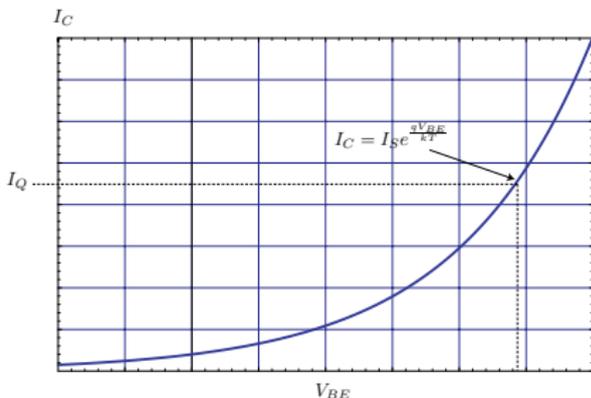For instance, for a BJT (Si, SiGe, GaAs) operated in forward-active region, the collector current is a smooth function of the voltage  $V_{BE}$




# BJT Distortion

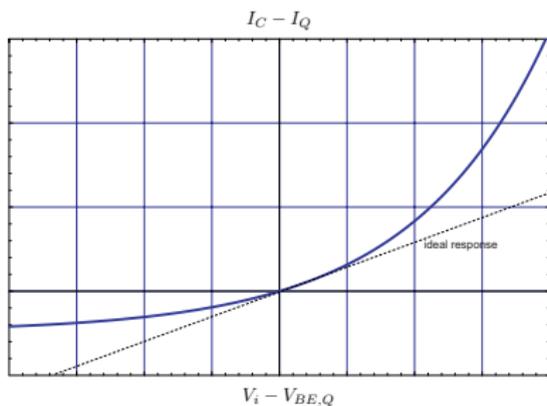

- We shift the origin by eliminating the DC signals,  $i_o = I_C - I_Q$ . The input signal is then applied around the DC level  $V_{BE,Q}$ .
- Note that an ideal amplifier has a perfectly linear line.

# JFET Distortion


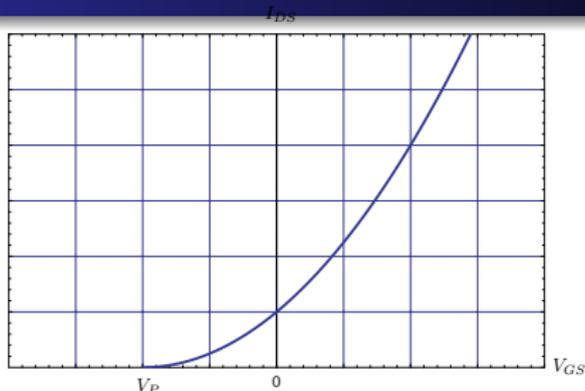


- JFETs are sometimes used in RF circuits. The I-V relation is also approximately square law

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

- The gate current (junction leakage) is typically very small  $I_G \sim 10^{12} \text{A}$ . So for all practical purposes,  $R_i = \infty$ .

# MOSFET Distortion

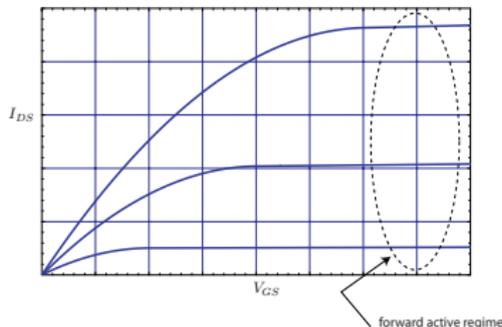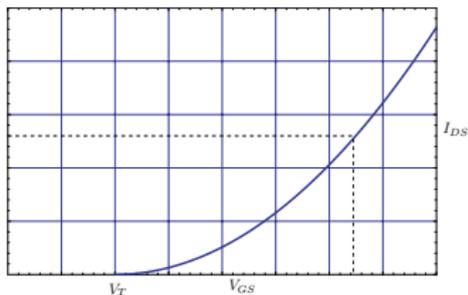

- The long-channel device also follows the square law relation (neglecting bulk charge effects)

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

- This is assuming the device does not leave the forward active (saturation) regime.

- Short-channel devices are even more difficult due to velocity saturation and field dependent mobility. A simple model for a transistor in forward active region is given by (neglecting output resistance)

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} \frac{(V_{GS} - V_t)^2}{1 + \theta(V_{GS} - V_t)}$$

- Note that the device operation near threshold is not captured by this equation.

# Single Equation MOSFET Model

- The I-V curve of a MOSFET in moderate and weak inversion is easy to describe in a “piece-meal” fashion, but difficult to capture with a single equation. One approximate single-equation relationship often used is given by


$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} \frac{X^2}{1 + \theta X}$$

where  $X$  is given by

$$X = 2\eta \frac{kT}{q} \ln \left( 1 + e^{\frac{q(V_{GS} - V_t)}{2\eta kT}} \right)$$

- If the exponential term dominates, then  $X = V_{GS} - V_t$ , which is true for operation in strong inversion. Otherwise,  $\ln(1 + a) \approx a$ , which makes the model mimic the weak-inversion “bipolar” exponential characteristic.

# Differential Pair

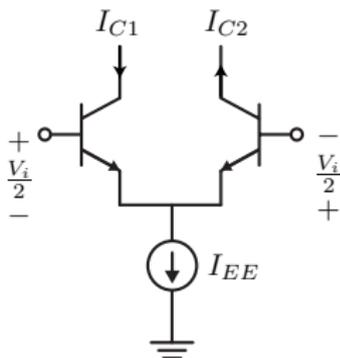


The differential pair is an important analog and RF building block.

- For a BJT diff pair, we have  $V_i = V_{BE1} - V_{BE2}$

$$I_{C1,2} = I_S e^{\frac{qV_{BE1,2}}{kT}}$$

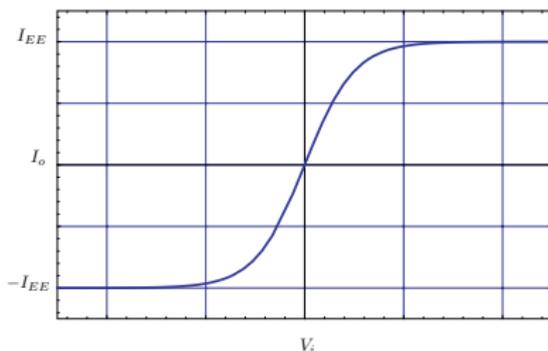- The sum of the collector currents are equal to the current source  $I_{C1} + I_{C2} = I_{EE}$



- The ideal BJT diff pair I-V relationship (neglecting base and emitter resistance) is given by

$$I_o = I_{C1} - I_{C2} = \alpha I_{EE} \tanh \frac{qV_i}{2kT}$$

- Notice that the output current saturates for large input voltages

## Modeling Amplifiers with a Power Series

# Power Series Relation

- For a general circuit, let's represent this behavior with a power series

$$s_o = a_1 s_i + a_2 s_i^2 + a_3 s_i^3 + \dots$$

- $a_1$  is the small signal gain
- The coefficients  $a_1, a_2, a_3, \dots$  are independent of the input signal  $s_i$  *but* they depend on bias, temperature, and other factors.

# Harmonic Distortion

- Assume we drive the amplifier with a time harmonic signal at frequency  $\omega_1$

$$s_i = S_1 \cos \omega_1 t$$

- A linear amplifier would output  $s_o = a_1 S_1 \cos \omega_1 t$  whereas our amplifier generates

$$s_o = a_1 S_1 \cos \omega_1 t + a_2 S_1^2 \cos^2 \omega_1 t + a_3 S_1^3 \cos^3 \omega_1 t + \dots$$


or

$$s_o = a_1 S_1 \cos \omega_1 t + \frac{a_2 S_1^2}{2} (1 + \cos 2\omega_1 t) + \frac{a_3 S_1^3}{4} (\cos 3\omega_1 t + 3 \cos \omega_1 t) + \dots$$

## Harmonic Distortion (cont)


- The term  $a_1 s_1 \cos \omega_1 t$  is the wanted signal.
- Higher harmonics are also generated. These are unwanted and thus called “distortion” terms. We already see that the second-harmonic  $\cos 2\omega_1 t$  and third harmonic  $\cos 3\omega_1 t$  are generated.
- Also the second order non-linearity produces a DC shift of  $\frac{1}{2} a_2 S_1^2$ .
- The third order generates both third order distortion and more fundamental. The sign of  $a_1$  and  $a_3$  determine whether the distortion product  $a_3 S_1^3 \frac{3}{4} \cos \omega_1 t$  adds or subtracts from the fundamental.
- If the signal adds, we say there is gain expansion. If it subtracts, we say there is gain compression.

## Second Harmonic Disto Waveforms

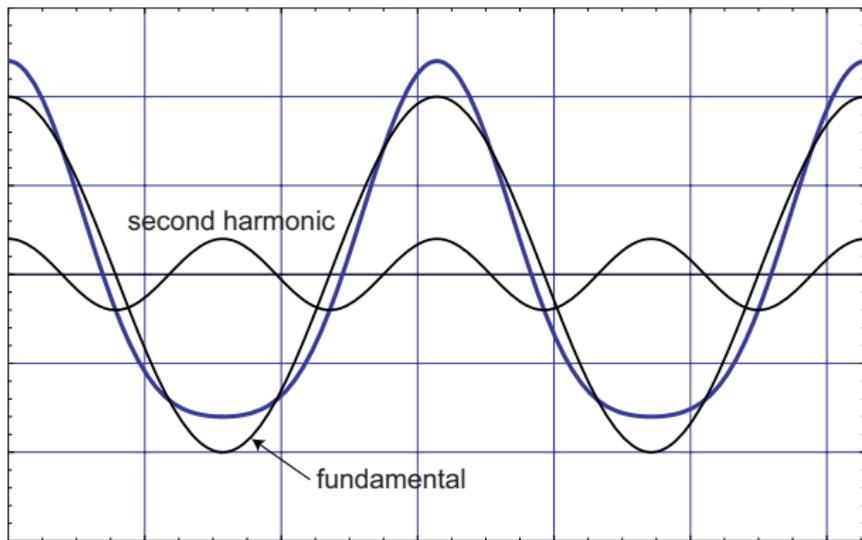


- The figure above demonstrates the waveform distortion due to second harmonic only.

# Third Harmonic Distortion Waveform

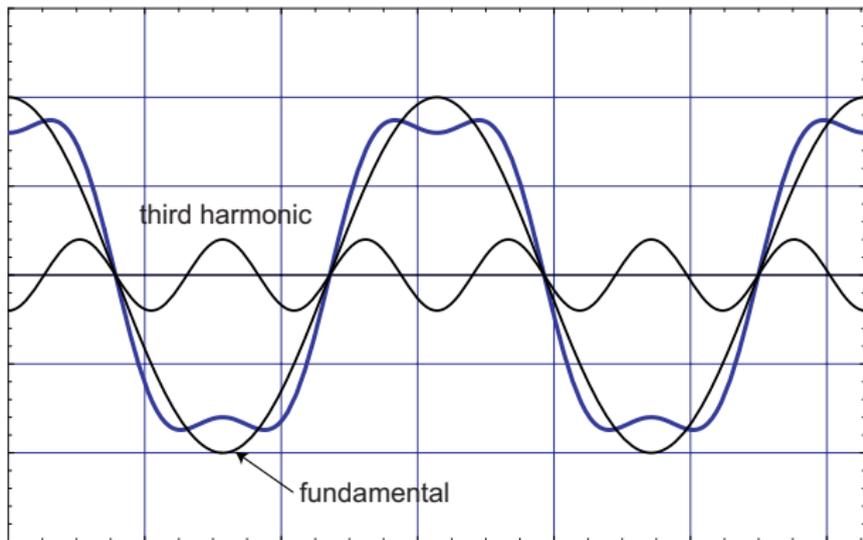

- The above figure shows the effects of the third harmonic, where we assume the third harmonic is in phase with the fundamental.

## Third Harmonic Waveform (cont)

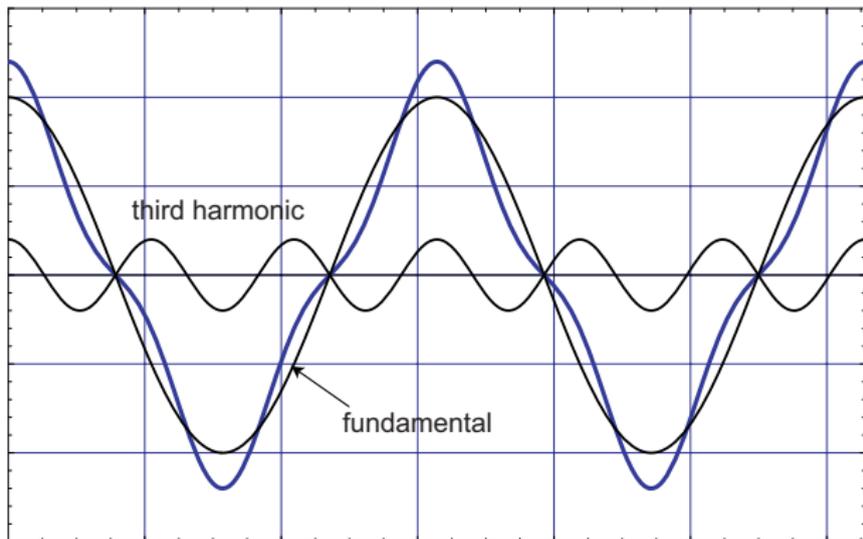

- The above figure shows the effects of the third harmonic, where we assume the third harmonic is out of phase with the fundamental.

# General Distortion Term

- Consider the term  $\cos^n \theta = \frac{1}{2^n} (e^{j\theta} + e^{-j\theta})^n$ . Using the Binomial formula, we can expand to

$$= \frac{1}{2^n} \sum_{k=0}^n \binom{n}{k} e^{jk\theta} e^{-j(n-k)\theta}$$

- For  $n = 3$

$$= \frac{1}{8} \left( \binom{3}{0} e^{-j3\theta} + \binom{3}{1} e^{j\theta} e^{-j2\theta} + \binom{3}{2} e^{j2\theta} e^{-j\theta} + \binom{3}{3} e^{j3\theta} \right)$$

$$= \frac{1}{8} (e^{-j3\theta} + e^{j3\theta}) + \frac{1}{8} 3 (e^{j\theta} + e^{-j\theta}) = \frac{1}{4} \cos 3\theta + \frac{3}{4} \cos \theta$$

## General Distortion Term (cont)

- We can already see that for an odd power, we will see a nice pairing up of positive and negative powers of exponentials
- For the even case, the middle term is the unpaired DC term

$$\binom{2k}{k} e^{jk\theta} e^{-jk\theta} = \binom{2k}{k}$$

- So only even powers in the transfer function can shift the DC operation point.
- The general term in the binomial expansion of  $(x + x^{-1})^n$  is given by

$$\binom{n}{k} x^{n-k} x^{-k} = \binom{n}{k} x^{n-2k}$$

## General Distortion Term (cont)

- The term  $\binom{n}{k}x^{n-2k}$  generates every other harmonic.
- If  $n$  is even, then only even harmonics are generated. If  $n$  is odd, likewise, only odd harmonics are generated.
- Recall that an “odd” function  $f(-x) = -f(x)$  (anti-symmetric) has an odd power series expansion

$$f(x) = a_1x + a_3x^3 + a_5x^5 + \dots$$


- Whereas an even function,  $g(-x) = g(x)$ , has an even power series expansion

$$g(x) = a_0 + a_2x^2 + a_4x^4 + \dots$$
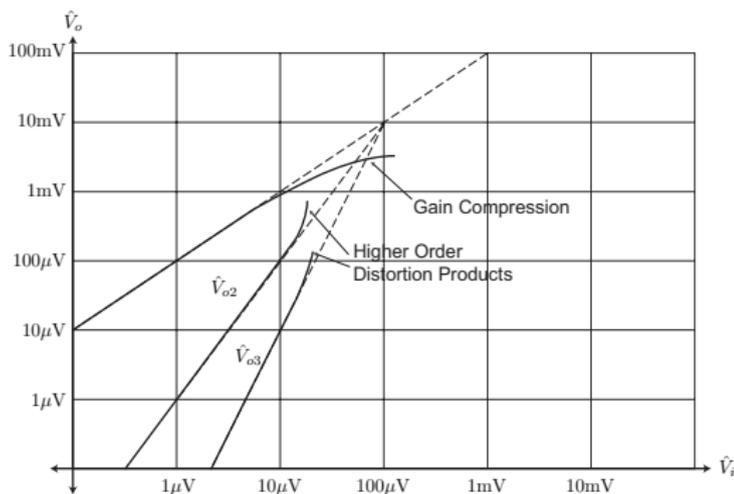
# Output Waveform

- In general, then, the output waveform is a Fourier series

$$v_o = \hat{V}_{o1} \cos \omega_1 t + \hat{V}_{o2} \cos 2\omega_1 t + \hat{V}_{o3} \cos 3\omega_1 t + \dots$$



## Harmonic Distortion Metrics

# Fractional Harmonic Distortion

- The fractional second-harmonic distortion is a commonly cited metric

$$HD_2 = \frac{\text{ampl of second harmonic}}{\text{ampl of fund}}$$

- If we assume that the square power dominates the second-harmonic

$$HD_2 = \frac{a_2 \frac{S_1^2}{2}}{a_1 S_1}$$

or

$$HD_2 = \frac{1}{2} \frac{a_2}{a_1} S_1$$

# Third Harmonic Distortion

- The fractional third harmonic distortion is given by

$$HD_3 = \frac{\text{ampl of third harmonic}}{\text{ampl of fund}}$$

- If we assume that the cubic power dominates the third harmonic

$$HD_3 = \frac{a_3 \frac{S_1^2}{4}}{a_1 S_1}$$

or

$$HD_3 = \frac{1}{4} \frac{a_3}{a_1} S_1^2$$

# Output Referred Harmonic Distortion

- In terms of the output signal  $S_{om}$ , if we again neglect gain expansion/compression, we have  $S_{om} = a_1 S_1$

$$HD_2 = \frac{1}{2} \frac{a_2}{a_1^2} S_{om}$$

$$HD_3 = \frac{1}{4} \frac{a_3}{a_1^3} S_{om}^2$$

- On a dB scale, the second harmonic increases linearly with a slope of one in terms of the output power whereas the third harmonic increases with a slope of 2.

- Recall that a general memoryless non-linear system will produce an output that can be written in the following form

$$v_o(t) = \hat{V}_{o1} \cos \omega_1 t + \hat{V}_{o2} \cos 2\omega_1 t + \hat{V}_{o3} \cos 3\omega_1 t + \dots$$

- By Parseval's theorem, we know the total power in the signal is related to the power in the harmonics

$$\begin{aligned} \int_T v^2(t) dt &= \int_T \sum_j \hat{V}_{oj} \cos(j\omega_1 t) \sum_k \hat{V}_{ok} \cos(k\omega_1 t) dt \\ &= \sum_j \sum_k \int_T \hat{V}_{oj} \cos(j\omega_1 t) \hat{V}_{ok} \cos(k\omega_1 t) dt \end{aligned}$$

- By the orthogonality of the harmonics, we obtain Parseval's  
Them

$$\int_T v^2(t) dt = \sum_j \sum_k \frac{1}{2} \delta_{jk} \hat{V}_{oj} \hat{V}_{ok} = \frac{1}{2} \sum_j \hat{V}_{oj}^2$$

- The power in the distortion relative to the fundamental power is therefore given by

$$\begin{aligned} \frac{\text{Power in Distortion}}{\text{Power in Fundamental}} &= \frac{V_{o2}^2}{V_{o1}^2} + \frac{V_{o3}^2}{V_{o1}^2} + \dots \\ &= HD_2^2 + HD_3^2 + HD_4^2 + \dots \end{aligned}$$

# Total Harmonic Distortion

- We define the *Total Harmonic Distortion* (*THD*) by the following expression

$$THD = \sqrt{HD_2^2 + HD_3^2 + \dots}$$

- Based on the particular application, we specify the maximum tolerable *THD*
- Telephone audio can be pretty distorted ( $THD < 10\%$ )
- High quality audio is very sensitive ( $THD < 1\%$  to  $THD < .001\%$ )
- Video is also pretty forgiving,  $THD < 5\%$  for most applications
- Analog Repeaters  $< .001\%$ . RF Amplifiers  $< 0.1\%$

## Intermodulation and Crossmodulation Distortion

# Intermodulation Distortion

- So far we have characterized a non-linear system for a single tone. What if we apply two tones

$$S_i = S_1 \cos \omega_1 t + S_2 \cos \omega_2 t$$

$$S_o = a_1 S_i + a_2 S_i^2 + a_3 S_i^3 + \dots$$

$$= a_1 S_1 \cos \omega_1 t + a_1 S_2 \cos \omega_2 t + a_2 (S_i)^2 + a_3 (S_i)^3 + \dots$$

- The second power term gives

$$a_2 S_1^2 \cos^2 \omega_1 t + a_2 S_2^2 \cos^2 \omega_2 t + 2a_2 S_1 S_2 \cos \omega_1 t \cos \omega_2 t$$

$$= a_2 \frac{S_1^2}{2} (\cos 2\omega_1 t + 1) + a_2 \frac{S_2^2}{2} (\cos 2\omega_2 t + 1) + \\ a_2 S_1 S_2 (\cos(\omega_1 + \omega_2)t - \cos(\omega_1 - \omega_2)t)$$

## Second Order Intermodulation

- The last term  $\cos(\omega_1 \pm \omega_2)t$  is the second-order intermodulation term
- The intermodulation distortion  $IM_2$  is defined when the two input signals have equal amplitude  $S_i = S_1 = S_2$

$$IM_2 = \frac{\text{Amp of Intermod}}{\text{Amp of Fund}} = \frac{a_2}{a_1} S_i$$

- Note the relation between  $IM_2$  and  $HD_2$

$$IM_2 = 2HD_2 = HD_2 + 6\text{dB}$$

## Practical Effects of $IM_2$

- This term produces distortion at a lower frequency  $\omega_1 - \omega_2$  and at a higher frequency  $\omega_1 + \omega_2$
- Example: Say the receiver bandwidth is from 800MHz – 2.4GHz and two unwanted interfering signals appear at 800MHz and 900MHz.
- Then we see that the second-order distortion will produce distortion at 100MHz and 1.7GHz. Since 1.7GHz is in the receiver band, signals at this frequency will be corrupted by the distortion.
- A weak signal in this band can be “swamped” by the distortion.
- Apparently, a “narrowband” system does not suffer from  $IM_2$ ? Or does it ?

- In a low-IF or direct conversion receiver, the signal is down-converted to a low intermediate frequency  $f_{IF}$
- Since  $\omega_1 - \omega_2$  can potentially produce distortion at low frequency,  $IM_2$  is very important in such systems
- Example: A narrowband system has a receiver bandwidth of 1.9GHz - 2.0GHz. A sharp input filter eliminates any interference outside of this band. The IF frequency is 1MHz
- Imagine two interfering signals appear at  $f_1 = 1.910\text{GHz}$  and  $f_2 = 1.911\text{GHz}$ . Notice that  $f_2 - f_1 = f_{IF}$
- Thus the output of the amplifier/mixer generate distortion at the IF frequency, potentially disrupting the communication.

- Now let's consider the output of the cubic term

$$a_3 s_i^3 = a_3 (S_1 \cos \omega_1 t + S_2 \cos \omega_2 t)^3$$

- Let's first notice that the first and last term in the expansion are the same as the cubic distortion with a single input

$$\frac{a_3 S_{1,2}^3}{4} (\cos 3\omega_{1,2} t + 3 \cos \omega_{1,2} t)$$

- The cross terms look like

$$\binom{3}{2} a_3 S_1 S_2^2 \cos \omega_1 t \cos^2 \omega_2 t$$

- Which can be simplified to


$$\begin{aligned}3 \cos \omega_1 t \cos^2 \omega_2 t &= \frac{3}{2} \cos \omega_1 t (1 + \cos 2\omega_2 t) = \\ &= \frac{3}{2} \cos \omega_1 t + \frac{3}{4} \cos(2\omega_2 \pm \omega_1)\end{aligned}$$

- The interesting term is the intermodulation at  $2\omega_2 \pm \omega_1$
- By symmetry, then, we also generate a term like

$$a_3 S_1^2 S_2 \frac{3}{4} \cos(2\omega_1 \pm \omega_2)$$

- Notice that if  $\omega_1 \approx \omega_2$ , then the intermodulation  $2\omega_2 - \omega_1 \approx \omega_1$

# Inband IM3 Distortion

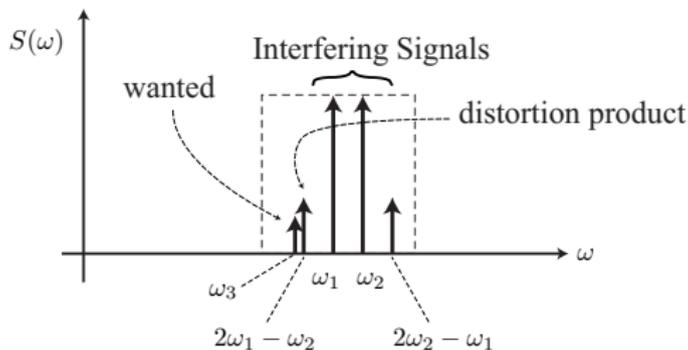

- Now we see that even if the system is narrowband, the output of an amplifier can contain in band intermodulation due to  $IM_3$ .
- This is in contrast to  $IM_2$  where the frequency of the intermodulation was at a lower and higher frequency. The  $IM_3$  frequency can fall in-band for two in-band interferer


- We define  $IM_3$  in a similar manner for  $S_i = S_1 = S_2$

$$IM_3 = \frac{\text{Amp of Third Intermod}}{\text{Amp of Fund}} = \frac{3 a_3}{4 a_1} S_i^2$$

- Note the relation between  $IM_3$  and  $HD_3$

$$IM_3 = 3HD_3 = HD_3 + 10\text{dB}$$


# Complete Two-Tone Response

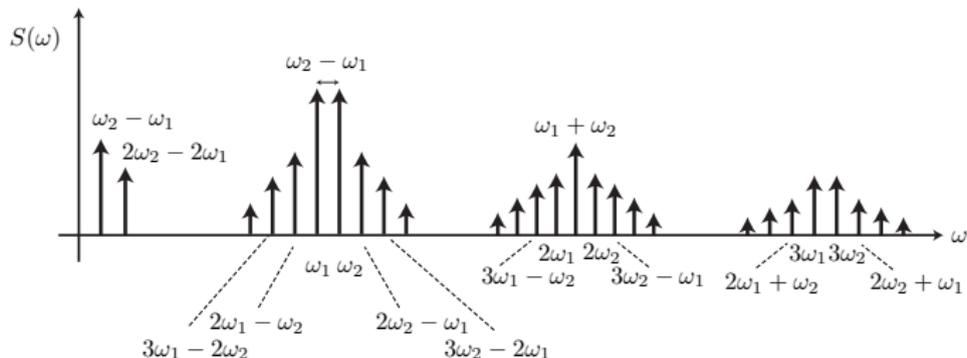

- We have so far identified the harmonics and  $IM_2$  and  $IM_3$  products
- A more detailed analysis shows that an order  $n$  non-linearity can produce intermodulation at frequencies  $j\omega_1 \pm k\omega_2$  where  $j + k = n$
- All tones are spaced by the difference  $\omega_2 - \omega_1$

## Examples

# Distortion of BJT Amplifiers

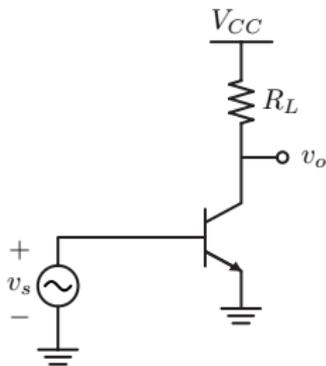

- Consider the CE BJT amplifier shown. The biasing is omitted for clarity.

- The output voltage is simply

$$V_o = V_{CC} - I_C R_C$$

- Therefore the distortion is generated by  $I_C$  alone. Recall that

$$I_C = I_S e^{qV_{BE}/kT}$$

## BJT CE Distortion (cont)

- Now assume the input  $V_{BE} = v_i + V_Q$ , where  $V_Q$  is the bias point. The current is therefore given by

$$I_C = \underbrace{I_S e^{\frac{V_Q}{V_T}}}_{I_Q} e^{\frac{v_i}{V_T}}$$

- Using a Taylor expansion for the exponential

$$e^x = 1 + x + \frac{1}{2!}x^2 + \frac{1}{3!}x^3 + \dots$$

$$I_C = I_Q \left( 1 + \frac{v_i}{V_T} + \frac{1}{2} \left( \frac{v_i}{V_T} \right)^2 + \frac{1}{6} \left( \frac{v_i}{V_T} \right)^3 + \dots \right)$$

## BJT CE Distortion (cont)

- Define the output signal  $i_c = I_C - I_Q$

$$i_c = \frac{I_Q}{V_T} v_i + \frac{1}{2} \left( \frac{q}{kT} \right)^2 I_Q v_i^2 + \frac{1}{6} \left( \frac{q}{kT} \right)^3 I_Q v_i^3 + \dots$$

- Compare to  $S_o = a_1 S_i + a_2 S_i^2 + a_3 S_i^3 + \dots$

$$a_1 = \frac{qI_Q}{kT} = g_m$$

$$a_2 = \frac{1}{2} \left( \frac{q}{kT} \right)^2 I_Q$$

$$a_3 = \frac{1}{6} \left( \frac{q}{kT} \right)^3 I_Q$$

## Example: BJT HD2

- For any BJT (Si, SiGe, Ge, GaAs), we have the following result

$$HD_2 = \frac{1}{4} \frac{q\hat{v}_i}{kT}$$

- where  $\hat{v}_i$  is the peak value of the input sine voltage
- For  $\hat{v}_i = 10\text{mV}$ ,  $HD_2 = 0.1 = 10\%$
- We can also express the distortion as a function of the output current swing  $\hat{i}_c$

$$HD_2 = \frac{1}{2} \frac{a_2}{a_1^2} S_{om} = \frac{1}{4} \frac{\hat{i}_c}{I_Q}$$


- For  $\frac{\hat{i}_c}{I_Q} = 0.4$ ,  $HD_2 = 10\%$

- Let's see the maximum allowed signal for  $IM_3 \leq 1\%$

$$IM_3 = \frac{3}{4} \frac{a_3}{a_1} S_1^2 = \frac{1}{8} \left( \frac{q\hat{v}_i}{kT} \right)^2$$

- Solve  $\hat{v}_i = 7.3\text{mV}$ . That's a pretty small voltage. For practical applications we'd like to improve the linearity of this amplifier.

# Example: Disto in Long-Ch. MOS

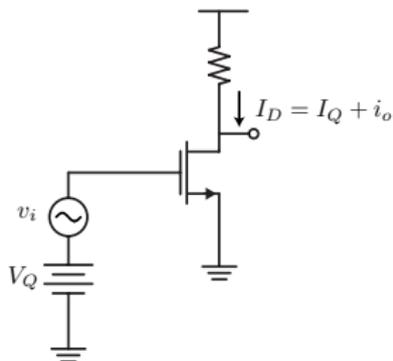

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$i_o + I_Q = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_Q + v_i - V_T)^2$$

- Ignoring the output impedance we have

$$= \frac{1}{2} \mu C_{ox} \frac{W}{L} \{ (V_Q - V_T)^2 + v_i^2 + 2v_i(V_Q - V_T) \}$$

$$= \underbrace{I_Q}_{\text{dc}} + \underbrace{\mu C_{ox} \frac{W}{L} v_i (V_Q - V_T)}_{\text{linear}} + \underbrace{\frac{1}{2} \mu C_{ox} \frac{W}{L} v_i^2}_{\text{quadratic}}$$

# Ideal Square Law Device

- An ideal square law device only generates 2nd order distortion

$$i_o = g_m v_i + \frac{1}{2} \mu C_{ox} \frac{W}{L} v_i^2$$

$$a_1 = g_m$$

$$a_2 = \frac{1}{2} \mu C_{ox} \frac{W}{L} = \frac{1}{2} \frac{g_m}{V_Q - V_T}$$



$$a_3 \equiv 0$$

- The harmonic distortion is given by

$$HD_2 = \frac{1}{2} \frac{a_2}{a_1} v_i = \frac{1}{4} \frac{g_m}{V_Q - V_T} \frac{1}{g_m} v_i = \frac{1}{4} \frac{v_i}{V_Q - V_T}$$

$$HD_3 = 0$$

# Real MOSFET Device

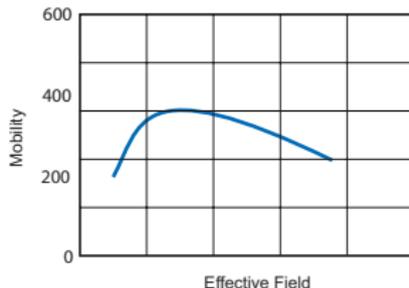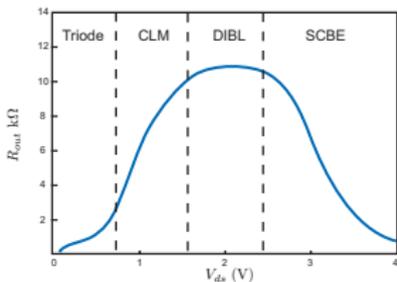

- The real MOSFET device generates higher order distortion
- The output impedance is non-linear. The mobility  $\mu$  is not a constant but a function of the vertical and horizontal electric field
- We may also bias the device at moderate or weak inversion, where the device behavior is more exponential
- There is also internal *feedback*